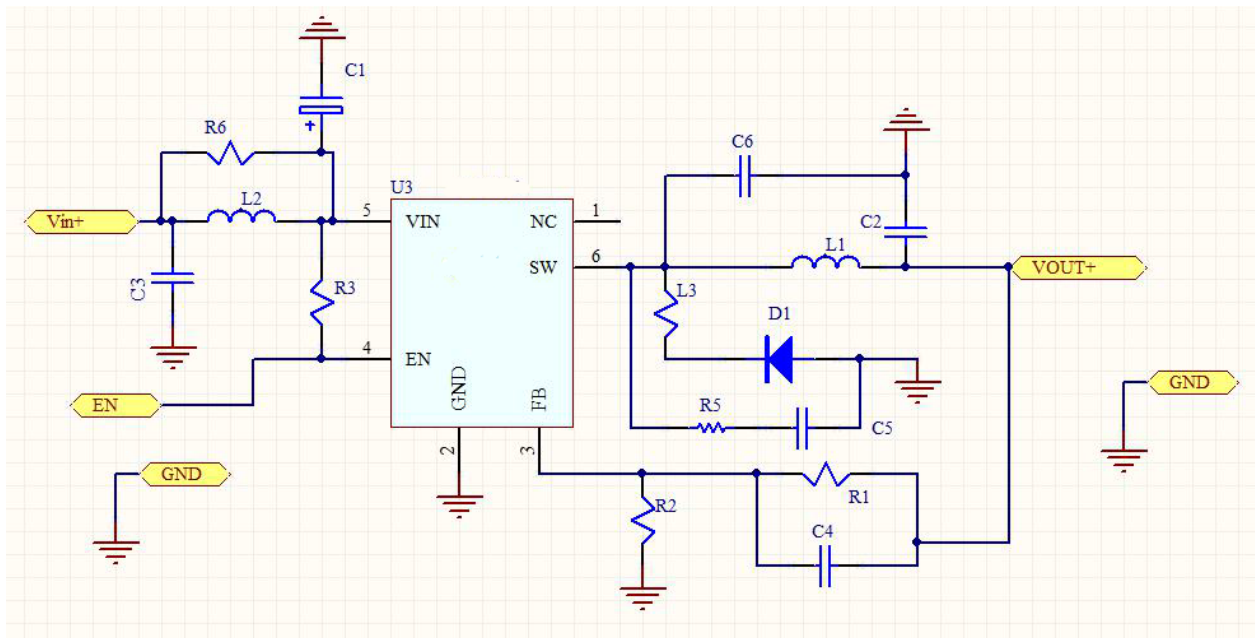





# 过传导辐射参考资料

## 1.典型应用原理图 $V_i=12-48V$ $V_o=5V$ $I_o=0.6A$


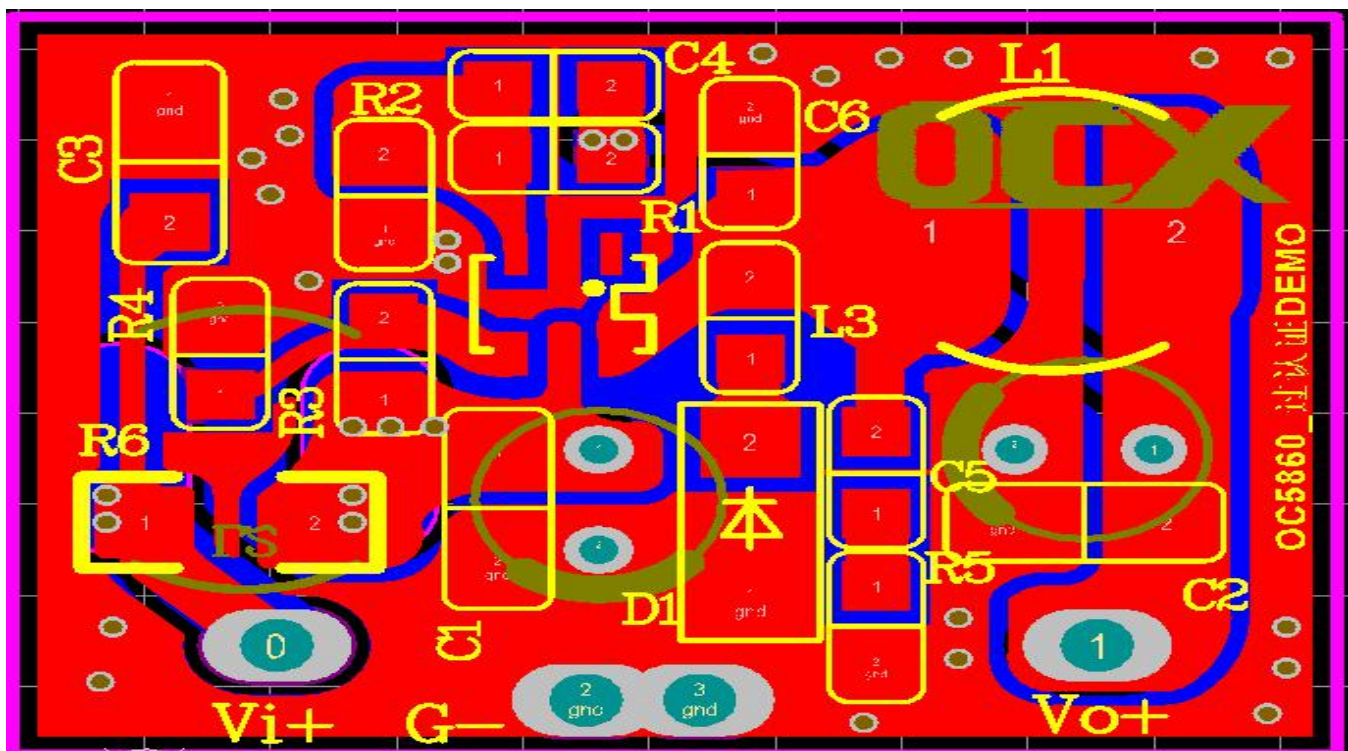
## 2.PCB 图 $V_i=12-48V$ $V_o=5V$ $I_o=0.6A$






### 3. BOM 清单 : $V_i=12-48V$ $V_o=5V$ $I_o=0.6A$


序号	材料名称	PCB-Layout 位号	技术规格	标准用量	价格
1	贴片电阻	R3	510K±5% 0805	1	
2	贴片电阻	R1	120K±5% 0805	1	
3	贴片电阻	R2	23.7K±5% 0805	1	
4	贴片电容	C4	47pF±10%/25V/X7R/0805	1	
5	贴片电容	C5	1nF±10%/25V/X7R/0805	1	
6	贴片电容	C6	470pF±10%/25V/X7R/0805	1	
7	贴片电容	C3	4.7uF±10%/50V/X7R/1206	1	
8	贴片电容	C2	22uF±10%/25V/X7R/1206	1	
9	插件电解	C1	22uF/100V	1	
10	电感	L1 L2	FNR6045-100uH	2	需要屏蔽电感
11	二极管	D1	SS260/60V/2A/SMA	1	
12	贴片磁珠	L3	磁珠阻抗1000ohm/0805/0.8A	1	
13	IC	U1	OC5860	1	

### 4. EMI 测试数据


$V_i=12V$   $V_o=5V$   $I_o=50mA$

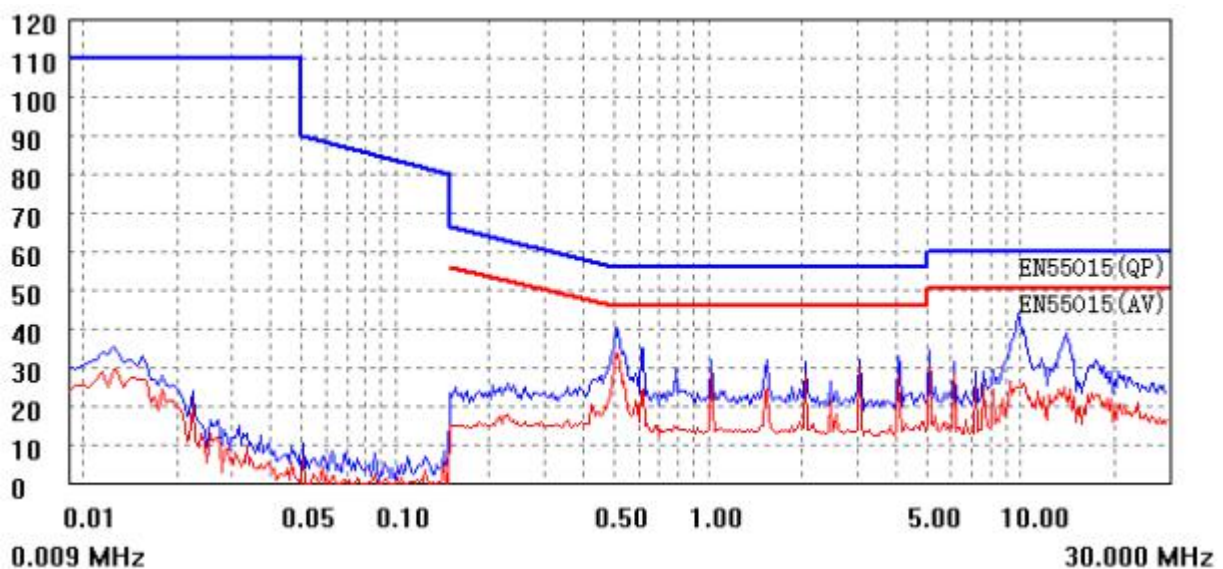


$V_i=12V$   $V_o=5V$   $I_o=100mA$

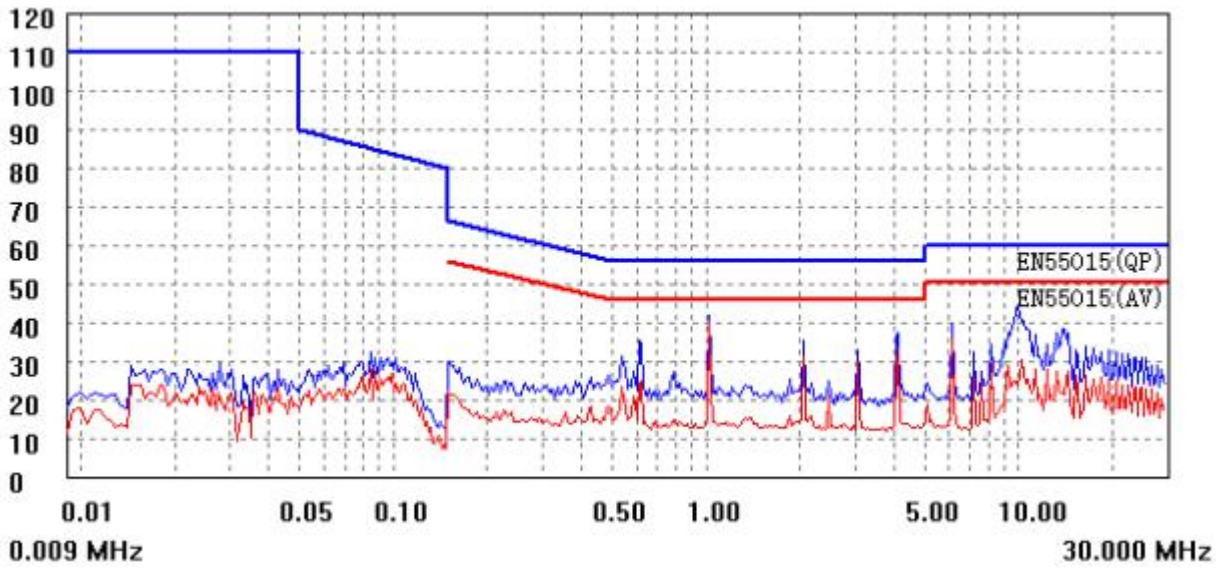

**Vi=12V Vo=5V Io=0.5A**

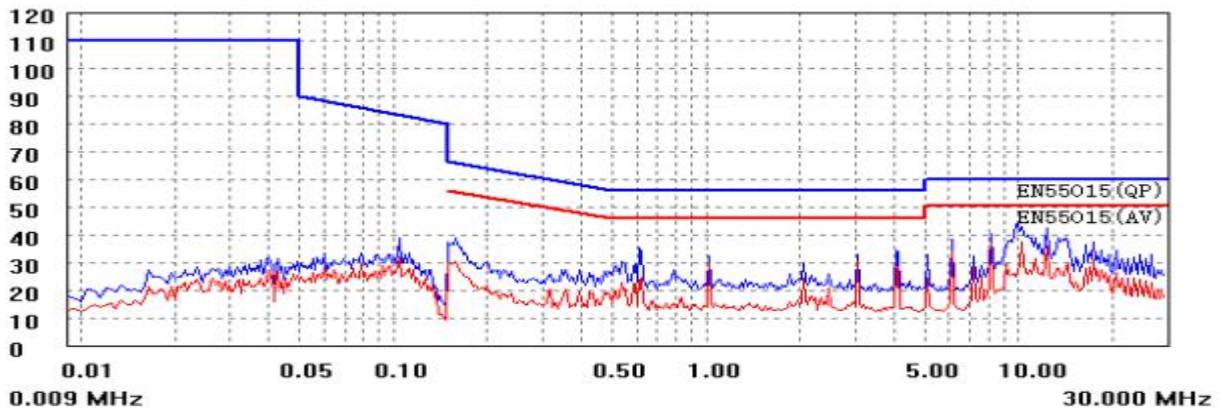


**Vi=48V Vo=5V Io=50mA**

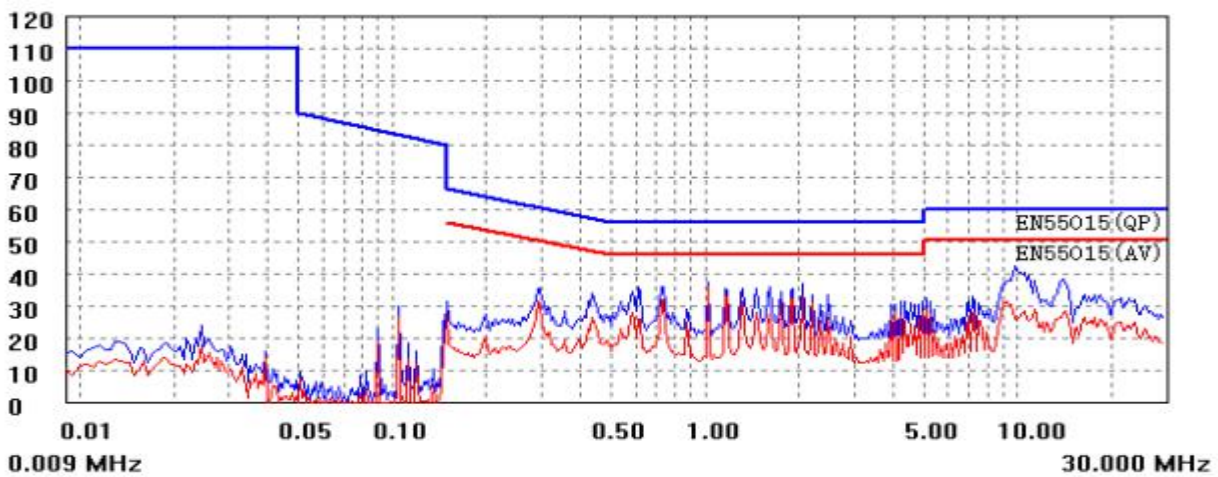






$V_i=48V$   $V_o=5V$   $I_o=100mA$

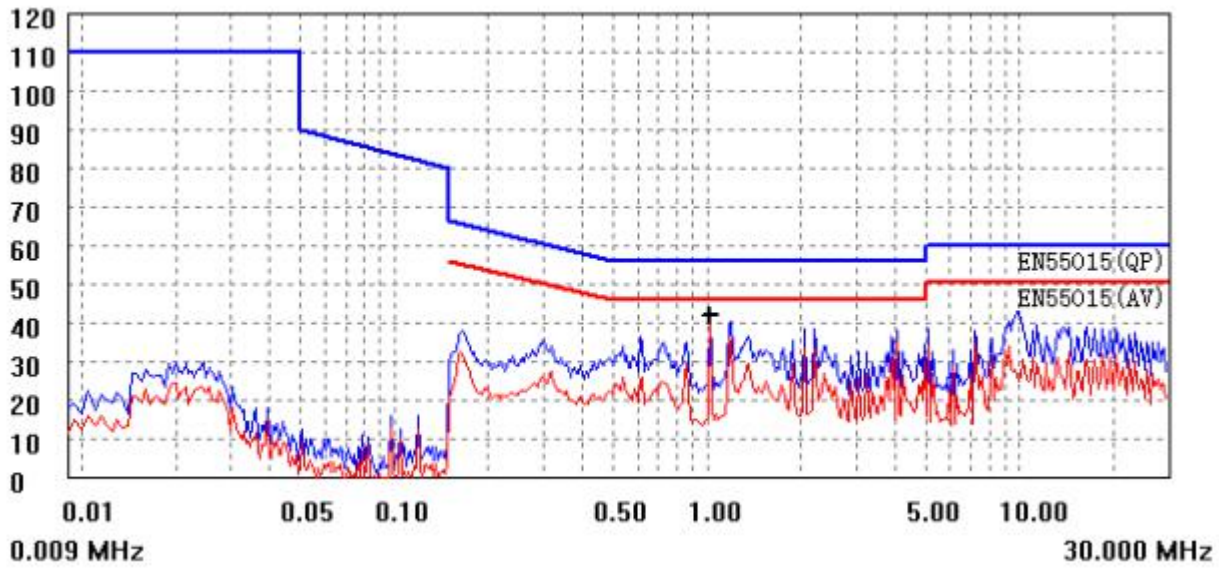


$V_i=48V$   $V_o=5V$   $I_o=0.5A$

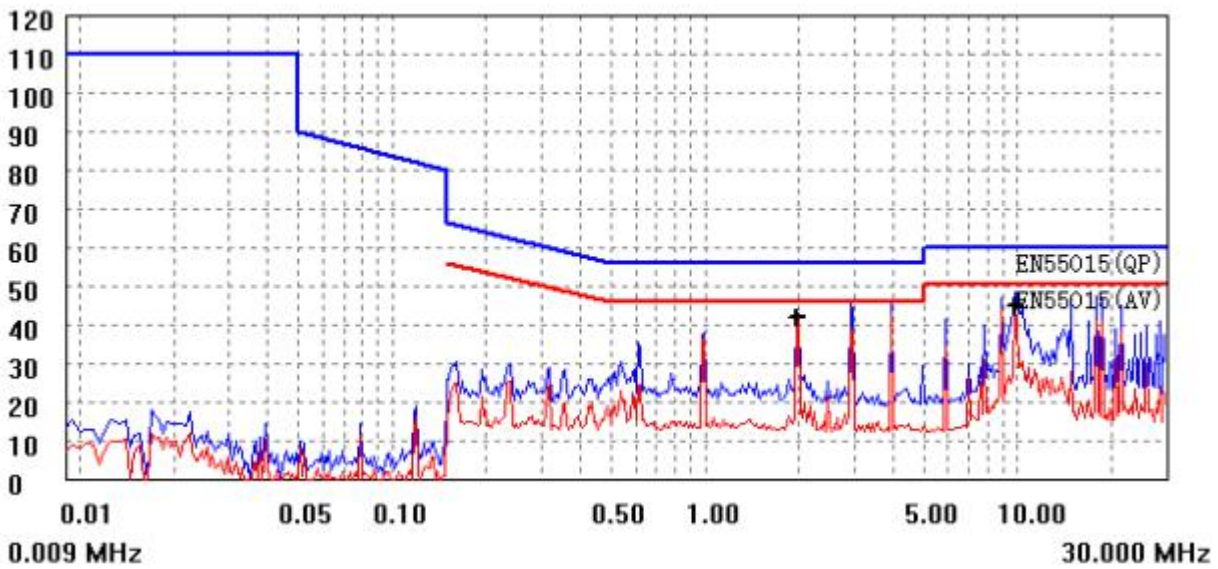




## 5. EMC 测试数据


$V_i=12V$   $V_o=5V$   $I_o=50mA$

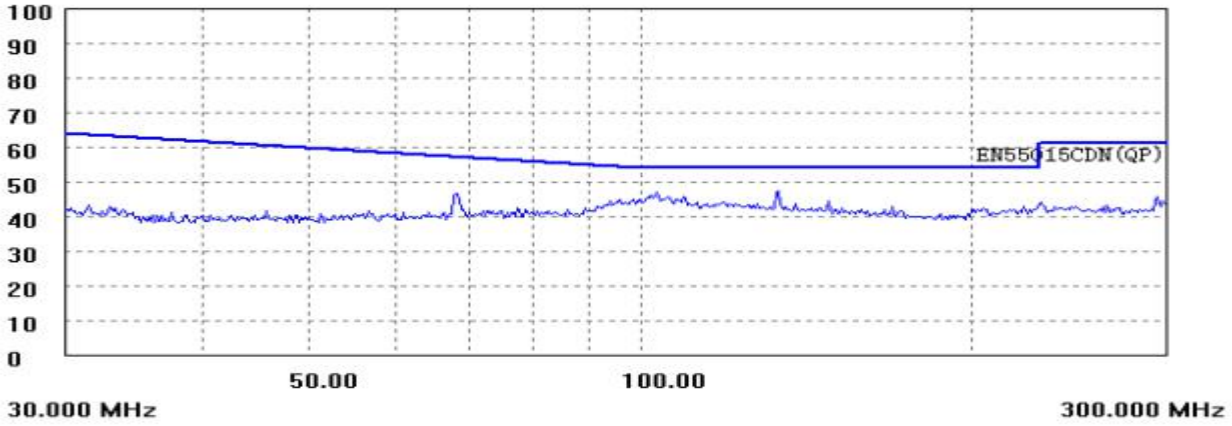

$V_i=12V$   $V_o=5V$   $I_o=100mA$

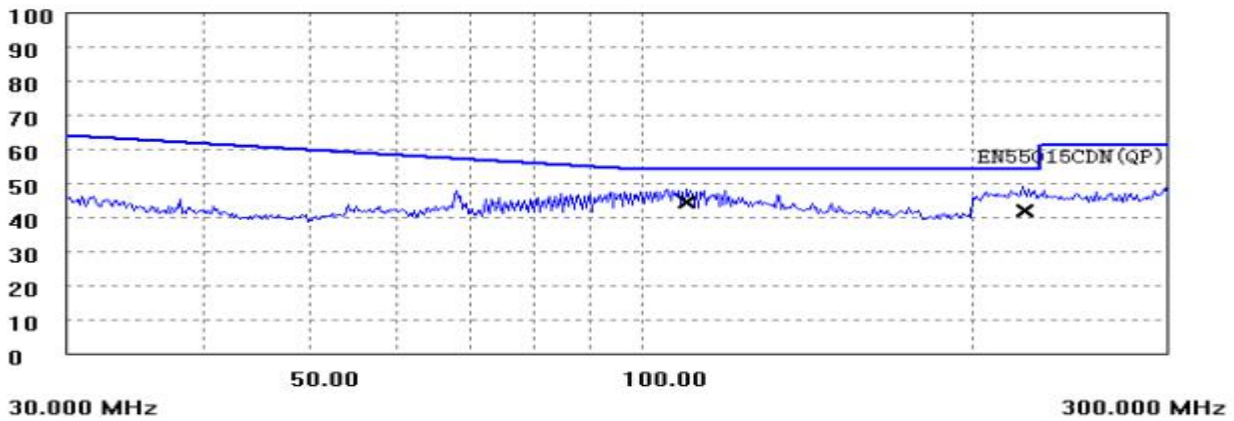


$V_i=12V$   $V_o=5V$   $I_o=0.5A$

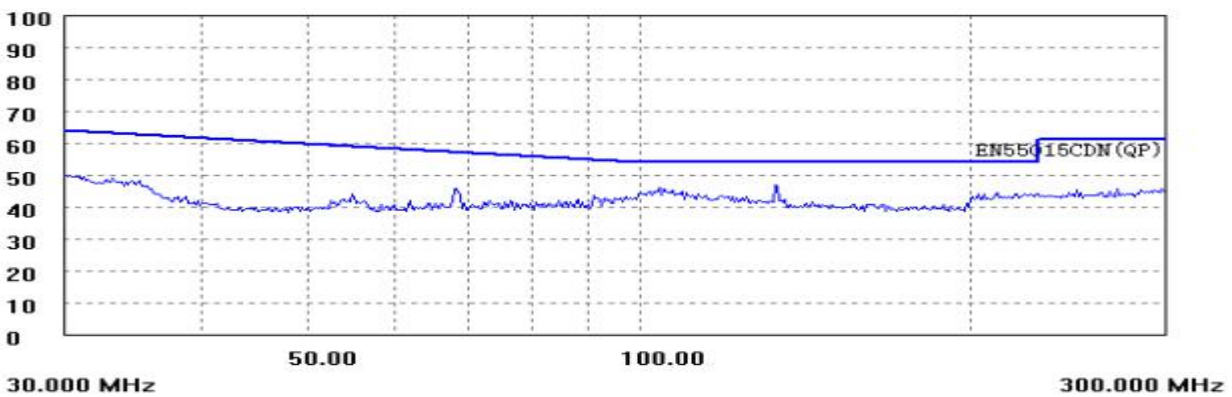





**$V_i=48V$   $V_o=5V$   $I_o=50mA$**

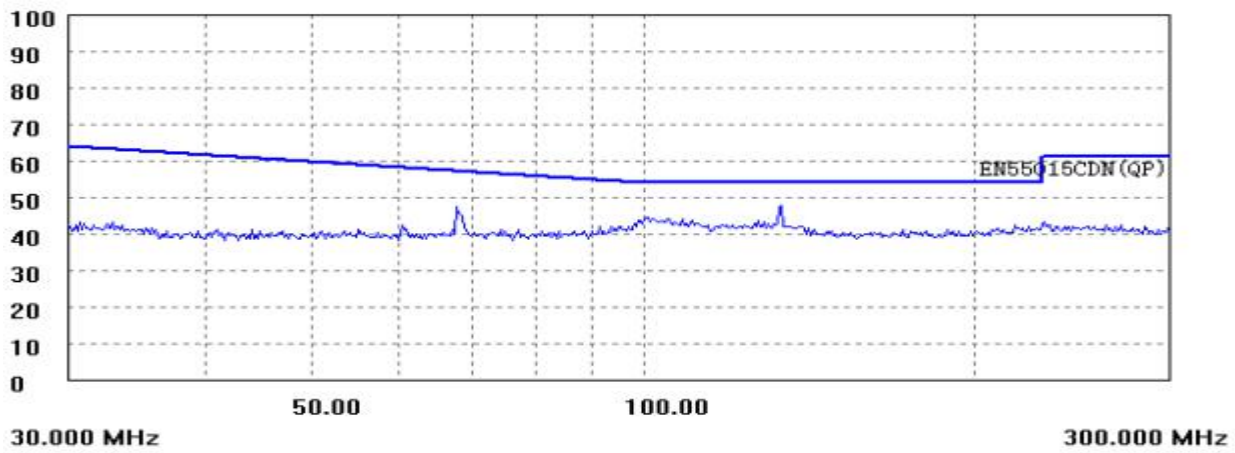

**$V_i=48V$   $V_o=5V$   $I_o=100mA$**

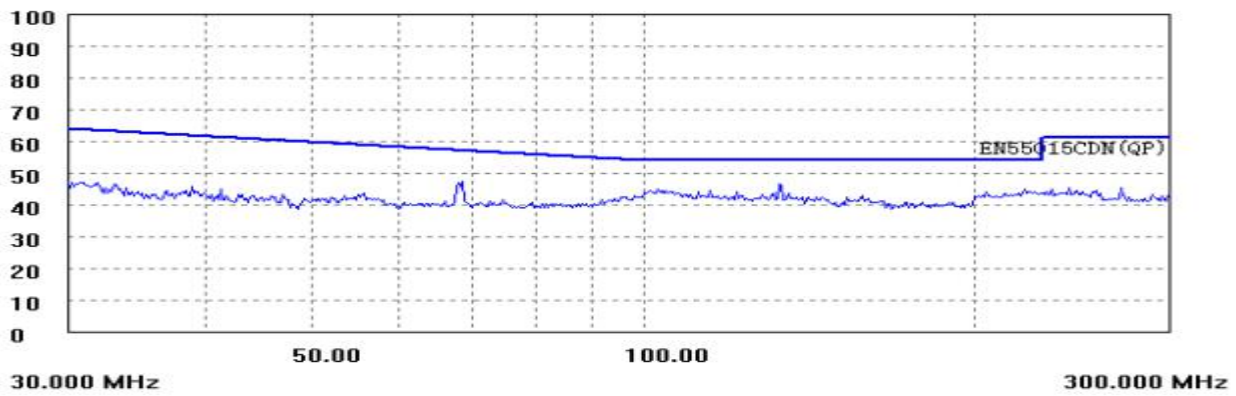


**$V_i=48V$   $V_o=5V$   $I_o=0.5A$**

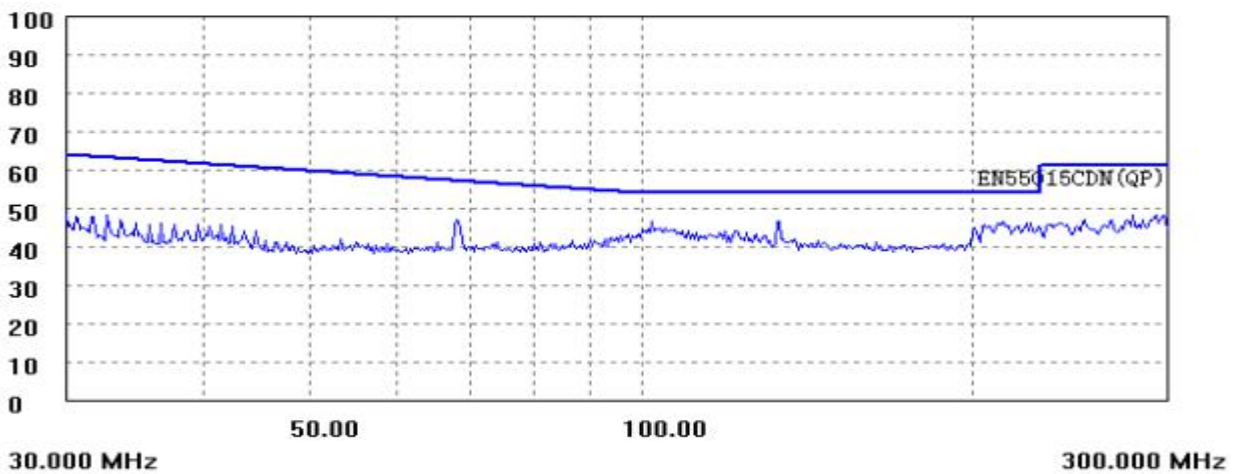




## 6.过传导辐射注意事项。


1. 输入端要加差模电感，电感量不要低于 33uH。

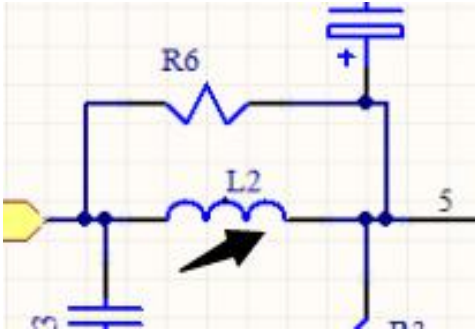

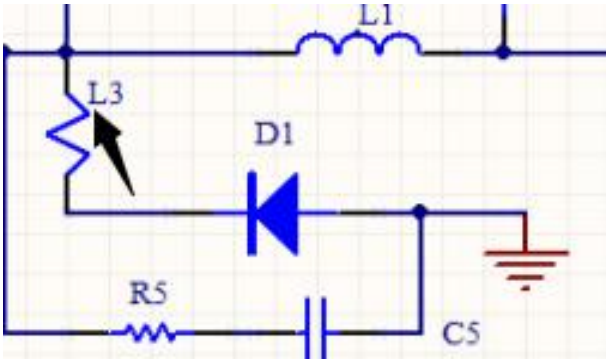2. 续流二极管负极串磁珠，磁珠阻抗为 500R-1000R，最好是 1000R。



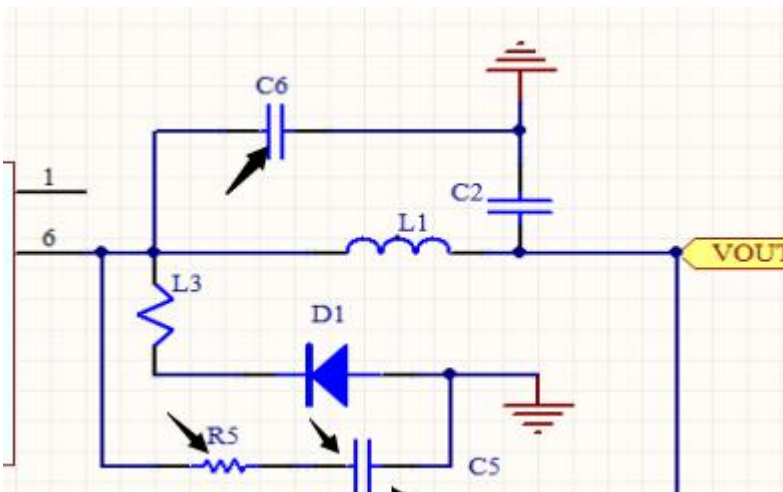3. 磁珠加电容吸收，续流二极管加 RC 吸收， $R=10-20R$ ， $C=1-2.2nF$ 。



4. 输入差模电感和功率电感用屏蔽型电感。
5. 在 Layout 时要注意控制大电流环路，环路越小越容易过传导辐射。